

# **DESIGN OF SERIES RESONANT DC-DC CONVERTER FOR EV BATTERY CHARGING**

Project Report submitted by,

Yaduraj Singh Tomar (231040124)

Ankit Kumar Maurya (231040019)

M.Tech (Power Engineering)

Under the guidance of  
Dr. Suvendu Samantha



**Design and Simulate a 1KW Series Resonant DC-DC Converter For EV Battery Charging**  
Input Voltage = 400V , Output Voltage = 48V,


Choose appropriate transformer turn ratio , Leakage Inductance, Switching Frequency etc.

Ignore Magnetizing Current


Topology :Full Bridge VSI And Full Bridge Diode Rectifier in the load side

Design a single loop control with appropriate SSE, Settling Time and the Phase Margin ,  
Show a Step

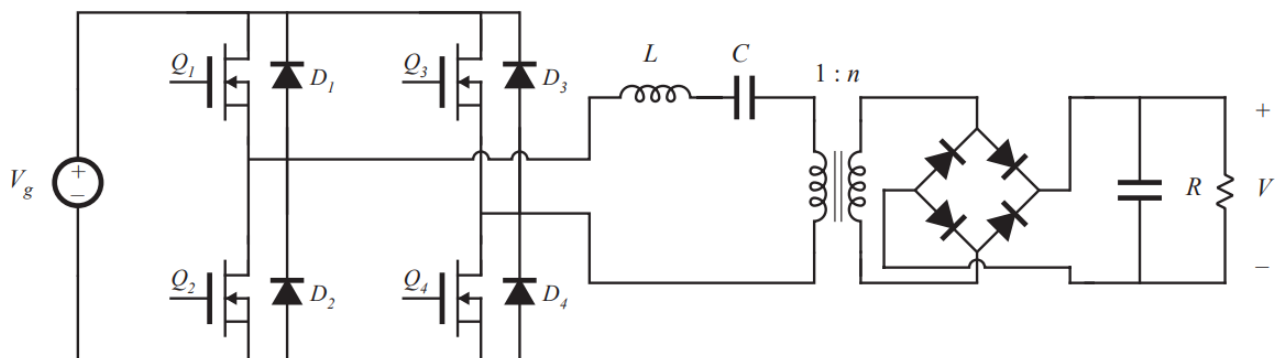Response in simulation and verify Settling time



## Matlab Model :

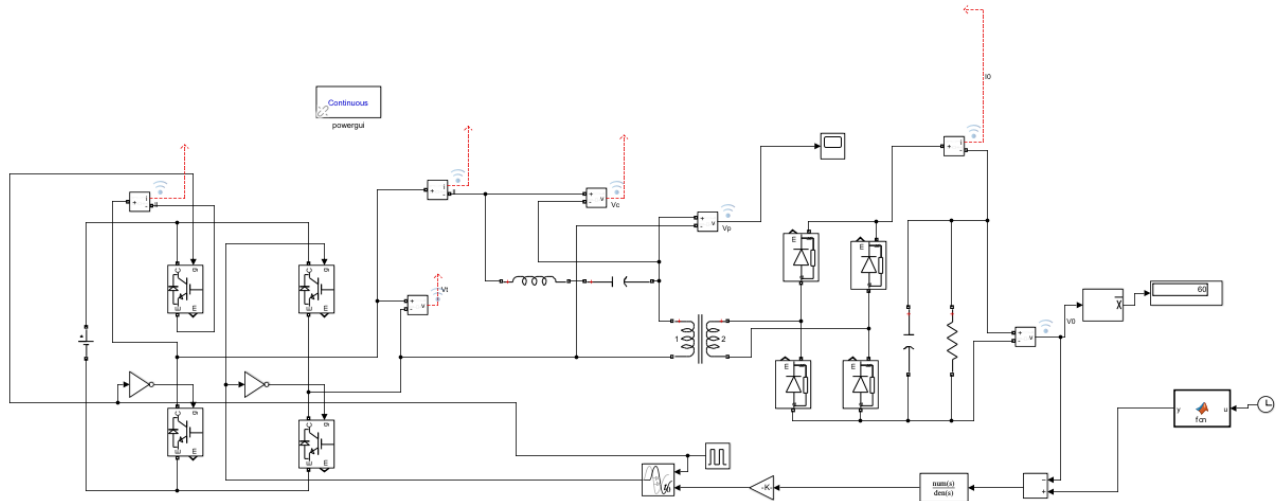

## Given Data :

$$V_g = 400\text{V}$$


$$V_o = 48\text{V}$$

$$P_o = 1000\text{W}$$

## Calculations :

Given data  $V_g = 400\text{ V}$ ,  $V_o = 48\text{ V}$ ,  $P_o = 1\text{ kW}$

DC-DC series resonant converter

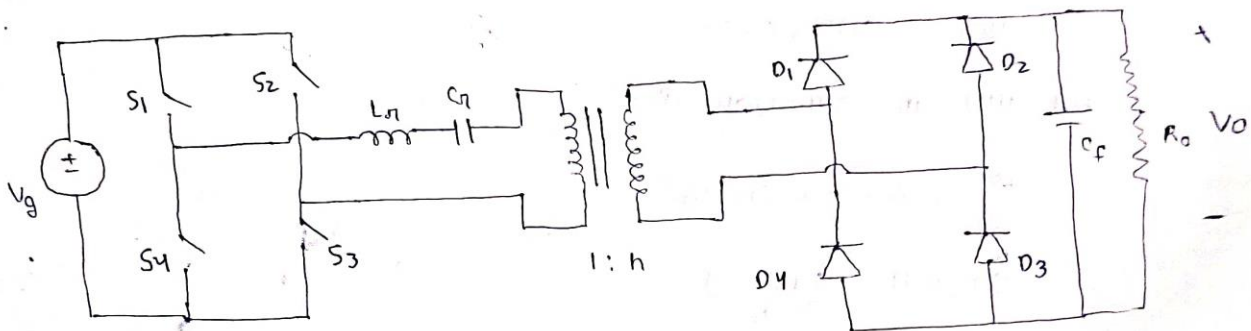

$$R = \frac{V_o^2}{P} = \frac{48 \times 48}{1000}$$

$$R = 2.304 \Omega$$

We know that DC voltage gain

$$\frac{V_o}{V_{avg}} = n H(s) \cdot \sin(\pi d)$$

$$\text{let } Q = 20, \quad f_{sw} = 100\text{ KHz}, \quad f_o = 98\text{ KHz}$$

$$\frac{V_o}{V_g} = n H(s) \cdot \sin(\pi d)$$

$$\frac{48}{400} = n \cdot H(s) \cdot \sin(\pi d) \quad \text{--- ①}$$

We know that

$$H(s) = \frac{\frac{s}{Q_e \omega_o}}{1 + \frac{s}{Q_e \omega_o} + \left(\frac{s}{\omega_o}\right)^2} = \frac{\frac{j100 \times 10^3 \times 2\pi}{20 \times 2\pi \times 98 \times 10^3}}{1 + \left(\frac{j100 \times 10^3 \times 2\pi}{20 \times 2\pi \times 98 \times 10^3}\right) + \left(\frac{j2\pi \times 100 \times 10^3}{2\pi \times 98 \times 10^3}\right)^2}$$

$$H(s) = \frac{\frac{j100}{20 \times 98}}{1 + \left(\frac{j100}{20 \times 98}\right) + \left(\frac{j100}{98}\right)^2}$$

$$H(s) = \frac{J0.05102}{1 + (J0.05102) - 1.0412}$$

$$= \frac{J0.05102}{-0.0412 + J0.05102}$$

$$H(s) = 0.778 \angle -38.92$$

Put  $H(s)$  in equation ①

$$\frac{48}{400} = 0.778 \cdot n \sin(\pi d)$$

$$\sin(\pi d) = \frac{0.15 + 24}{n}$$

$$\text{Let } n = 0.4$$

$$\sin(\pi d) = \frac{0.15 + 24}{0.4} = 0.3856$$

$$\pi d = \sin^{-1}(0.3856)$$

$$d = 0.126$$

$$\text{As } Q_e = \frac{\omega_o L \cdot n^2}{R_e}$$

$$L = \frac{Q_e \cdot R_e}{\omega_o \cdot n^2}$$

$$L = \frac{20 + 1.86944}{(0.4)^2 + 2\pi \times 98 \times 10^3}$$

$$L = 379.4 \mu\text{H}$$

$$\omega_o = \frac{1}{\sqrt{LC}} \quad C = \frac{1}{\omega_o^2 L}$$

$$C = \frac{1}{(2\pi \times 98 \times 10^3)^2 + 379.4 \times 10^{-6}}$$

$$C = 6.676 \times 10^{-9} \text{ F}$$

$$\frac{\tilde{V}_o(s)}{\tilde{d}(s)} = \frac{\tilde{V}_{s1}}{\tilde{d}} \cdot \frac{\tilde{I}_{n1}}{\tilde{V}_{s1}} \cdot \frac{\tilde{V}_o}{\tilde{I}_{n1}}$$

↑  
Inverter  
TIF
↑  
Tank  
TIF
← Rectifier  
TIF


$\frac{\tilde{V}_o(s)}{\tilde{d}(s)}$  is plant transfer function.

①  $\frac{\tilde{V}_{s1}}{\tilde{d}} = 4V_g \cos(\pi d) = 4 \times 400 \times \cos(\pi \times 0.121) = 1476.276$  — (ii)

② For  $\frac{\tilde{I}_{n1}}{\tilde{V}_{s1}}$

$$\frac{\tilde{I}_{n1}}{\tilde{V}_{s1}} = \frac{\tilde{V}_{n1}}{\tilde{V}_{s1}} \cdot \frac{\tilde{I}_{n1}}{\tilde{V}_{n1}}$$

$$= \frac{R_e}{\left| R_e + sL + \frac{1}{sc} \right|} \cdot \frac{1}{R_e}$$

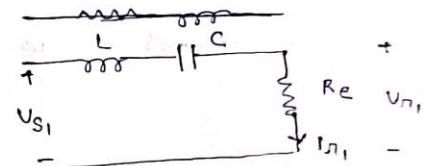

$$\frac{\tilde{I}_{n1}}{\tilde{V}_{s1}} = \frac{1}{R_e + sL + \frac{1}{sc}} = \frac{1}{Z_{in}}$$

$$= \frac{1}{1.878 + (j2\pi \times 100 \times 10^3 + 379.4 \times 10^6) + \frac{1}{(j2\pi \times 100 \times 10^3 \times 6.676 \times 10^{-9})}}$$

$$= \frac{1}{1.878 + j238.384 - j238.3986}$$

$$= \frac{1}{(1.878 - j0.0146)}$$


$$\frac{\tilde{I}_{n1}}{\tilde{V}_{s1}} = 0.5324 \angle 0.445 \text{ — (iii)}$$

Switching Frequency = 628 Krad/s


$\omega_{gc} < \text{Switching Frequency}/10$

● (iii) Rectifier
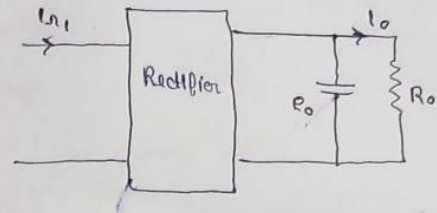
$$\frac{V_o(s)}{I_{n1}(s)} = \frac{2/\pi}{(sC + 1/R_o)}$$



O/P capacitor design -

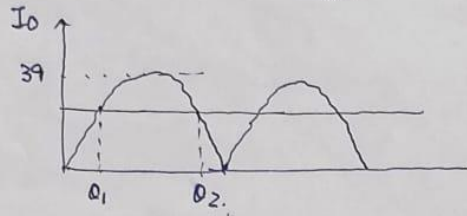

$$I_o(\text{avg}) = \frac{V_o}{R_o} = \frac{40}{2.304} = 20.833$$

$$\theta_2 = \pi - \theta_1$$

$$\text{For } \theta_1: 39 \sin \omega t - 20.833 = 0$$

$$39 \sin \omega t = 20.833$$

$$\theta_1 = 0.6595$$

$$\theta_2 = 2.48$$

Now we know that

$$Q = C \cdot \Delta V$$

$$Q = \frac{1}{2\omega} \int_{\theta_1}^{\theta_2} (39 \sin \omega t - 20.833) d(\omega t)$$

$$= \frac{1}{2\pi \times 900 \times 10^3} \left[ \int_{0.6595}^{2.48} 39 \sin \omega t d(\omega t) - \int_{0.6595}^{2.48} 20.833 d(\omega t) \right]$$

$$= \frac{1}{2\pi \times 900 \times 10^3} \left[ 39 \left[ \cos 2.48 - \cos 0.6595 \right] - 20.833 (2.48 - 0.6595) \right]$$

$$= \frac{1}{2\pi \times 900 \times 10^3} [53.6966 - 37.93]$$

$$Q = \frac{15.766}{2\pi \times 900 \times 10^3} = C \Delta V$$

$$\Delta V = 0.48$$

$$C = \frac{15.766}{2\pi \times 900 \times 10^3 \times 0.48}$$

$$C = 26.15 \mu F \approx 30 \mu F$$



We have taken  $C = 100 \mu F$  to minimise ripple.

$$\frac{V_o(s)}{I_{in}(s)} = \frac{0.6366}{s(100 \times 10^{-6}) + 0.4340}$$

$$\text{New Plant TIF} = 4V_g \cos(\pi f) \cdot \frac{1}{\left[ R_e + sL + \frac{1}{sC} \right]} \cdot \frac{2/\pi}{(sC + 1/R_o)^{1/2}}$$

Putting all values of eq. (ii), (iii) and (iv)

$$T(s) = 1476.276 \times 0.532 (0.4 + s) \cdot \frac{2/\pi}{(sC + 1/R_o)^{1/2}}$$

$$T(s) = \frac{500.617 (0.4 + s)}{s(100 \times 10^{-6}) + 0.4340}$$

④ For Settling time  $\leq 5ms$

$$T_s \leq 5ms$$

$$\frac{\eta}{\omega_{gc}} \leq 5ms$$

$$\omega_{gc} \geq 200 \text{ rad/s}$$

also

$$\omega_{crossover} = 62.8 \text{ k rad/s}$$

$$\omega_{gc} < 62.8 \text{ k rad/s}$$

$$200 < \omega_{gc} < 62.8 \text{ k}$$

$$\text{We have taken } \omega_{gc} = 9.1 \times 10^3 \text{ rad/s}$$

Also  $\omega_{gc}$  for uncompensated system is

$$\omega_{crossover} = 5.01 \times 10^6 \text{ rad/s}$$

So we have to Reduce  $\omega_{gc}$  for this we

have used PI Controller



We added first Integrator at origin to reduce steady state error and  $\omega_{gc}$

Now our transfer function become

$$T_1(s) = \frac{500 \cdot 617}{s(100 \times 10^6) + 0.4340} + \frac{K_i}{s}$$

after this we are getting  $\omega_{gc} = 1.12 \times 10^3 \text{ rad/s}$

we want to make our desired cross over at  $9.1 \text{ Krad/s}$  so we added Proportional controller  
overall, we added PI Controller

we added a zero at  $\omega = 1500 \text{ rad/s}$

So our transfer function become

$$T_2(s) = \frac{500 \cdot 617}{s(100 \times 10^6) + 0.4340} \cdot \frac{K_i}{s} \cdot \left( \frac{s + 1500}{1500} \right)$$

Now at  $\omega_{gc} = 9.1 \times 10^3 \text{ rad/s}$

$$|GH| = |T_2| = 1 \quad \text{at } \omega = 9.1 \times 10^3$$

$$\Rightarrow \left| \frac{500 \cdot 617}{j(9.1 \times 10^3)(100 \times 10^6) + 0.4340} \cdot \frac{K_i}{(j \times 9.1 \times 10^3)} \cdot \left( \frac{j \times 9.1 \times 10^3}{1500} + 1 \right) \right| = 1$$


on solving, we get

$$K_i = 3$$


Overall Transfer function

$$|GH| = \left( \frac{1501 \cdot 851}{8(100 \times 10^6) + 0.4340} \right) \frac{1}{s} \left( 1 + \frac{s}{1500} \right)$$


## Bode Plot Of Uncompensated System :

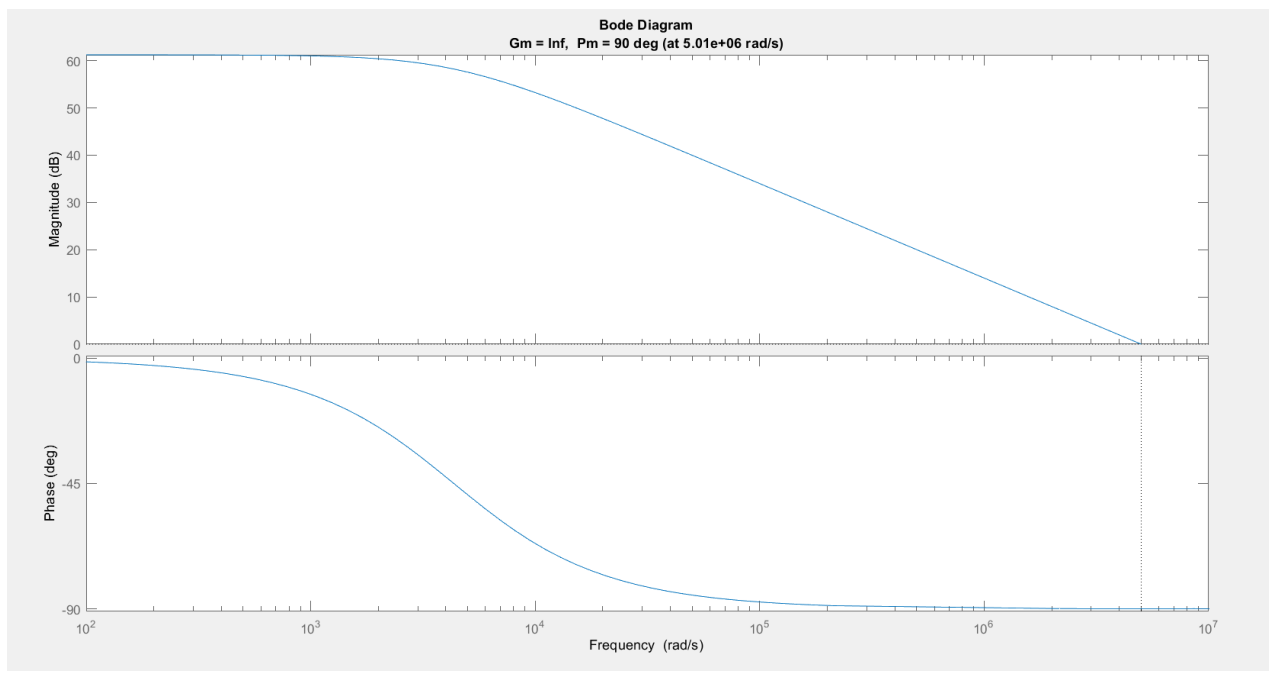

## Bode Plot of Compensator :

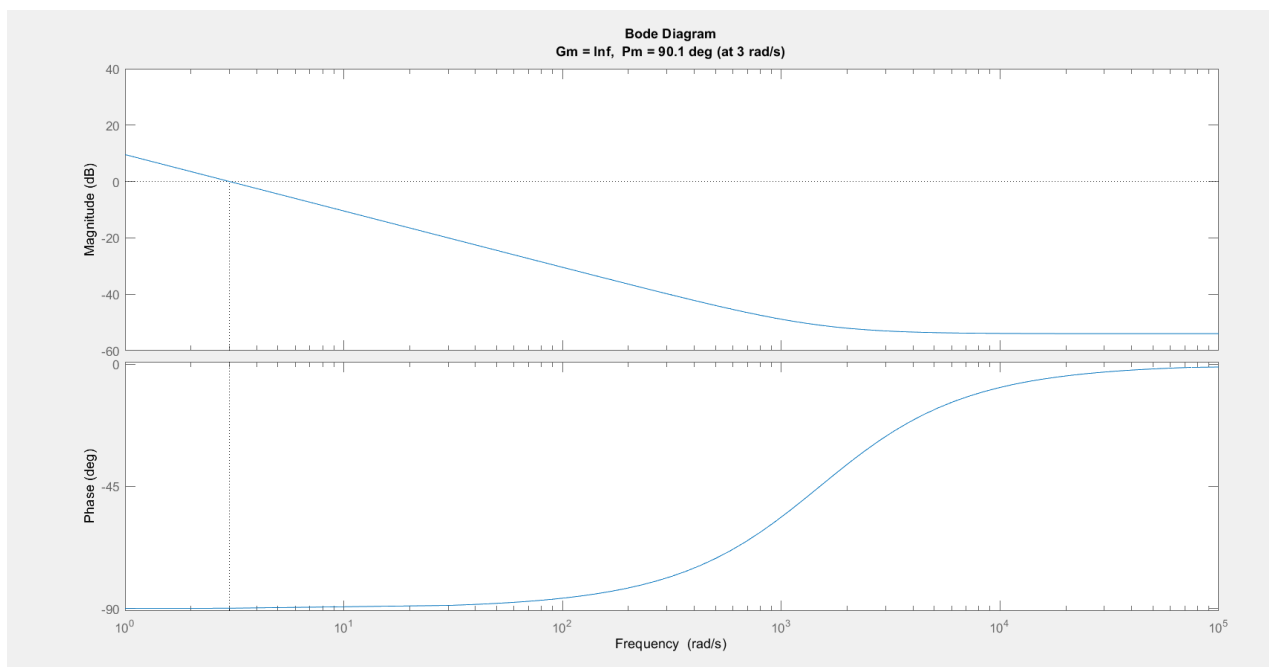


## Bode Plot of Compensated System:

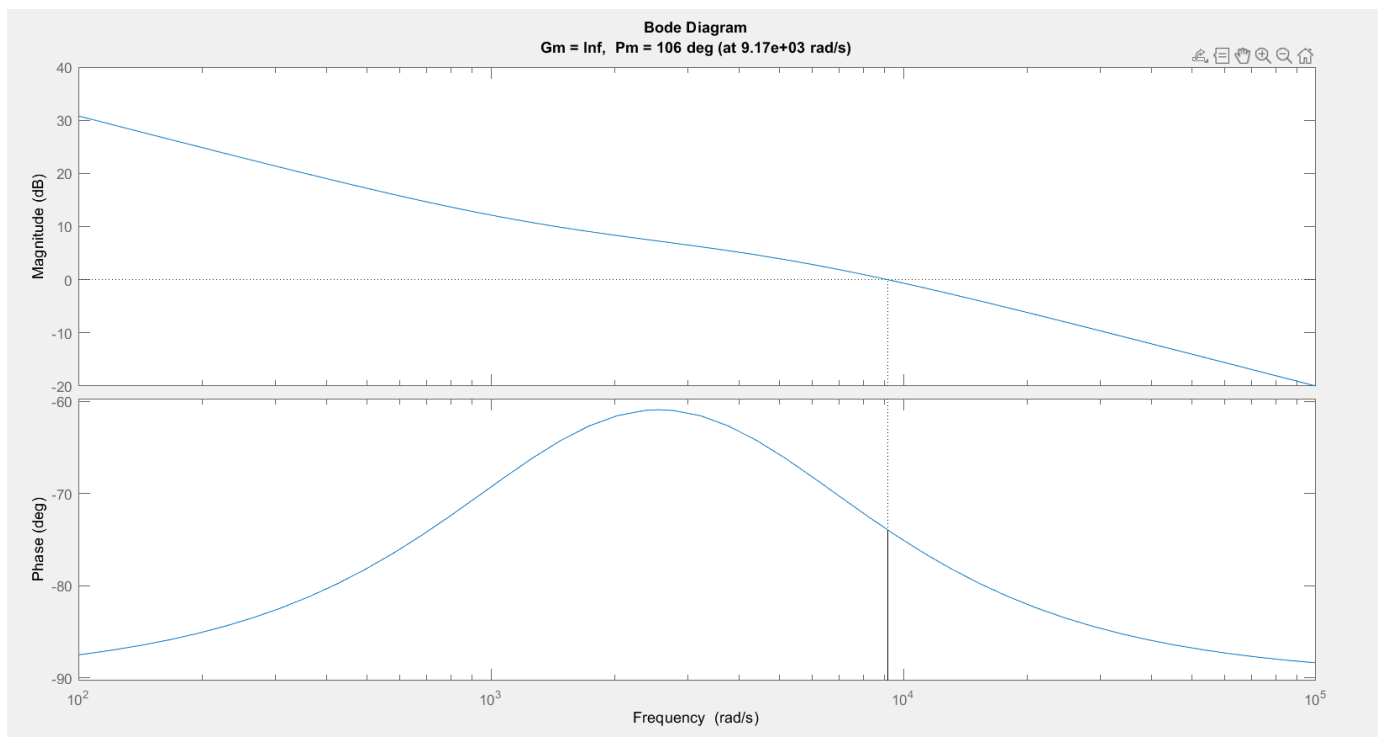


- In the Compensated system we are having Cross over at  $9.17 \times 10^3$  rad/sec
- And we are getting Phase Margin = 106 degree
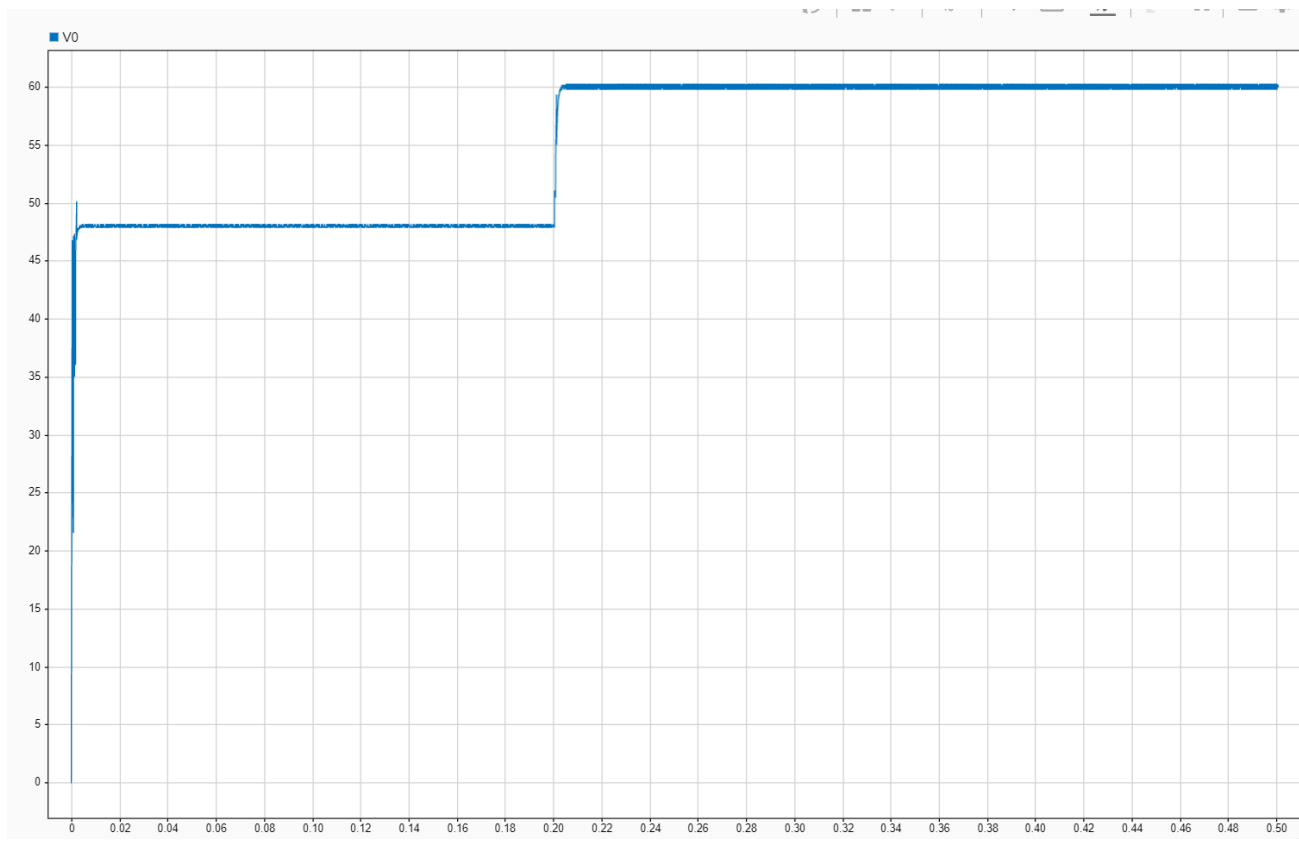
## Output Voltage of Series Resonant DC- DC Converter

After application of step input at 0.2s :



## Output Current (Io) :

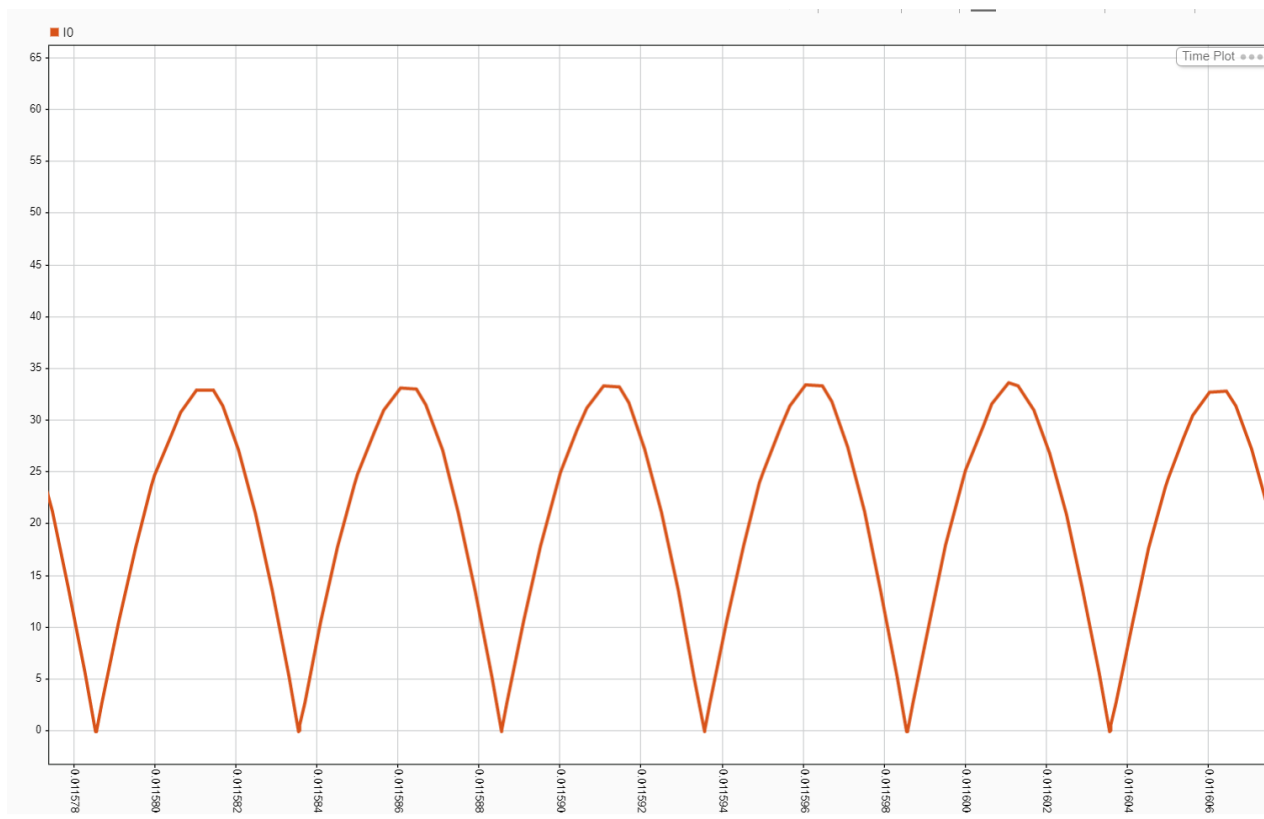

## **Switch Ratings :**

### **For Mosfet :**

- RMS Current Rating = 6.65A
- Voltage Rating = 400V
- RMS Current Rating Taken = 13.3A Safety factor =2)
- Voltage rating Taken = 600V (Safety Factor =1.5)
- Hyperlink for Datasheet :  
[https://www.mouser.in/datasheet/2/196/Infineon\\_IPB65R190CFD7A\\_DataSheet\\_v02\\_01\\_EN-3362448.pdf](https://www.mouser.in/datasheet/2/196/Infineon_IPB65R190CFD7A_DataSheet_v02_01_EN-3362448.pdf)

### **For Diode :**

- Average Current Rating = 13.375A
- Voltage Rating = 60 V
- Average Current Rating = 20.6A Safety factor =1.5)
- Voltage rating Taken = 90V (Safety Factor =1.5)
- Hyperlink for Datasheet :  
<https://www.taiwansemi.com/assets/datasheet/pdf.php?pn=SRS2090>

## Final Results :

As overall TIF is type-1, For unit step I/P, steady

Steady state error ( $e_{ss}$ ) = 0

### Result:

①  $V_{in} = 400V$

①  $V_o = 48V$

① Step applied at 0.25 of 60V (48+12V)

①  $f_{sw} = 100kHz$

①  $f_{resonant} = 90kHz$

①  $n = 0.4$

①  $L_r = 379.94\mu H$

①  $C_r = 6.676nF$

①  $C_o = 100\mu F$

① Ripples in output voltage

① Before  $t < 0.25$ ,  $V_o = 48V$  - without step

$$\Delta V_o = 48.12 - 47.88 = 0.24 \text{ (Peak to Peak)}$$

② After  $t > 0.25$ ,  $V_o = 48+12V = 60V$  - with step

$$\Delta V_o = 60.20 - 59.82 = 0.38V \text{ (Peak to Peak)}$$

①



